AMRITA VISHWA VIDYAPEETHAM

DEEMED TO BE UNIVERSITY UNDER SECTION 3 OF THE UGC ACT, 1956

AMRITA SCHOOL OF ENGINEERING, BENGALURU

DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

B. TECH. V SEMESTER (ECE AND EAC) AY 2026-2027

ASSIGNMENT FOR 23ECE302 VLSI DESIGN

SYSTEM DESIGN FOR 23ECE383 VLSI DESIGN LABORATORY

REPORT

JULY TO NOVEMBER 2026

Implementation of a Compact Multiphase Divide-by-Two CMOS Frequency Divider in 45 nm CMOS (Cadence GPDK045)

Submitted by

REGISTER NUMBER	*NAME*	*SIGNATURE WITH DATE*

BATCH NUMBER: _____

_____

FACULTY EXAMINER SIGNATURE WITH EVALUATION DATE

TITLE OF THE SYSTEM DESIGN PROJECT:

Implementation of a Compact Multiphase Divide-by-Two CMOS Frequency Divider in 45 nm CMOS (Cadence GPDK045)

TITLE OF THE PAPER:

A Compact Multiphase Divide-by-Two CMOS Frequency Divider

DETAILS OF THE PAPER (SOURCE OF THE TITLE):

Authors: Yue-Fang Kuo, Shih-Hung Lin, Bo-Yi Chen and Liang-Chen Liu

Journal: IEEE Microwave and Wireless Technology Letters

Volume: 35

Issue: 5

Pages: 617-620

Date: May 2025

DOI: 10.1109/LMWT.2025.3528863

CIRCUIT DIAGRAM:

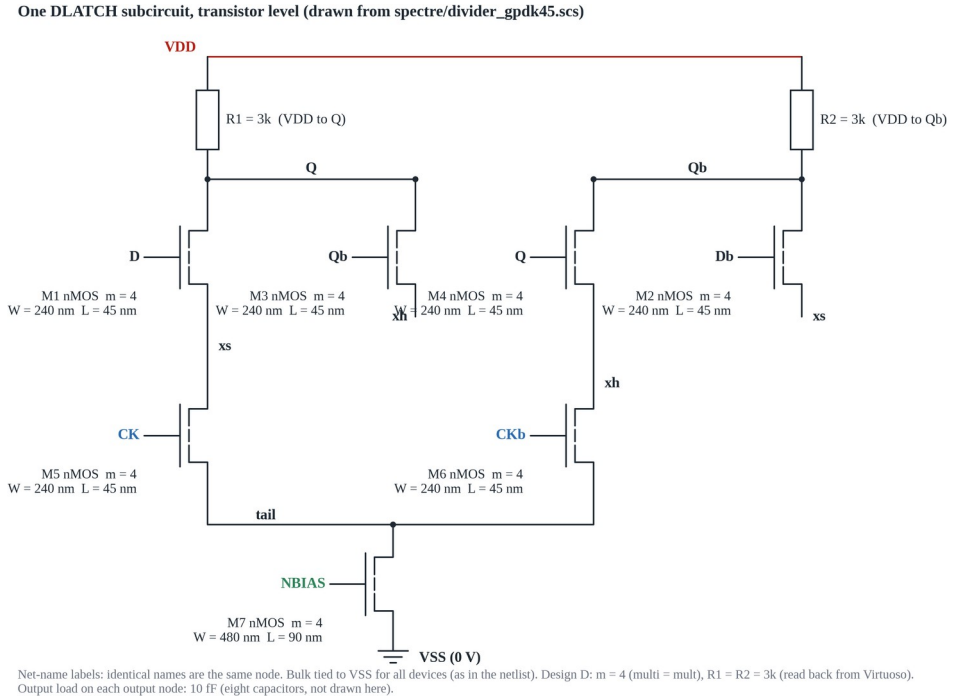


Figure 1: Schematic of the differential D-latch (DLATCH) stage (M1-M7, R1, R2). Sizing: M1-M6 W = 240 nm, L = 45 nm; M7 W = 480 nm, L = 90 nm. Values shown for design D (sized, m = 4, R1 = R2 = 3 kOhm, 1.4 GHz); unsized baseline uses multiplier m = 1, R = 8 kOhm.

THEORY AND WORKING PRINCIPLE:

Topology. The divider consists of four differential D-latches (DLATCH) connected in a ring with alternating cross-connections (Q1b-D2, Q2-D3, Q3b-D4, Q4-D1b) and inverted clocks on latches 2 and 3 (Kuo et al.). Each latch contains differential sampling pair M1-M2, clock switches M5-M6, regenerative cross-coupled pair M3-M4, tail current source transistor M7, and resistive loads R1-R2. Sampling occurs when input clock CK is high, and regeneration occurs when complementary clock CKb is active, producing eight phases at half the input frequency.

Elmore delay model. Latch propagation delay is modeled as t_pd = (8C)(R/2) = 4RC, where each output carries capacitance 8C and load R/2 = R1. Division requires half-period timing budget T_CK/2 > 2 Td, where Td is the single-latch propagation delay. For load capacitance C_L = 10 fF, the parasitic-free lower bound Td >= R1 C_L yields 30 ps for design D (sized, m = 4, R1 = R2 = 3 kOhm, 1.4 GHz) and 20 ps for design B (m = 4, R1 = R2 = 2 kOhm, 6 GHz). Timing budget T_CK/2 > 2 Td is met at 1.4 GHz (2 Td >= 60 ps vs 357 ps) and 6 GHz (2 Td >= 40 ps vs 83 ps). Design B divides up to 6 GHz and fails at 6.2 GHz (T_CK/2 = 80.6 ps); measured CK-to-Q1 delay (66.10 ps) is 3.3x the intrinsic bound (79% of T_CK/2), showing parasitic capacitance limits high-frequency operation.

Stack resistance and regeneration. The pull-down network forms a three-transistor stack (M1, M5, M7) with effective resistance 3 Ron/m, where Ron is the channel on-resistance and m is the device multiplier. Regeneration requires a loop gain gm R1 > 1 (gm is the transconductance), giving R1 >= 1.1 x (3 Ron/m). With Ron = 2.3 kOhm, the unit stack is 6.90 kOhm, requiring R1 >= 7.59 kOhm. Reference paper sizing (1.15 kOhm) falls below this threshold, preventing division. Measured thresholds for m = 1 span 6-7 kOhm at tail bias vb = 1 V and 7-8 kOhm at vb = 0.8 V. For m = 4, the required threshold is 1.90 kOhm (band 1.88-2.25 kOhm); design D (R1 = 3 kOhm) provides margin, while design B (R1 = 2 kOhm) operates within the marginal band. Measured division agrees with the rule for 5 of 5 tested parameter pairs. Unit device aspect ratio W/L = 5.33 (240 nm / 45 nm) matches the reference design ratio of 5.00 (0.9 um / 180 nm).

Phase-step relationship. Outputs toggle in pairs separated by t_pair (measured between rising edges of Q2 and Q3b), yielding alternating phase steps of a = 180 t_pair f_in degrees and (90 - a) degrees. For design D at 1.4 GHz, t_pair = 25.95 ps gives steps of 83.46 and 6.54 deg (a = 180 x 25.95 ps x 1.4 GHz = 6.54 deg). For design B at 6 GHz, t_pair = 38.16 ps gives 48.78 and 41.22 deg (a = 41.22 deg). The unsized baseline at 1.4 GHz gives 71.42 and 18.59 deg (t_pair = 73.75 ps, a = 18.59 deg). Nominal 45 deg spacing requires T_CK = 4 t_pair: 103.8 ps (9.63 GHz) for design D and 152.7 ps (6.55 GHz) for design B. Phase error decreases toward the divider limit, matching the reference benchmark (3.75 deg) in design B at 6 GHz.

Definitions of performance metrics. Propagation delay is the average time from each CK rising edge to the next transition across any output (25.99 ps for design D; single-edge CK-to-Q1 delay is 51.95 ps). Power is VDD times average supply current over full clock cycles. Power-delay product (PDP) is power times delay (fJ). Division is confirmed when all eight outputs toggle at f_in/2 within 0.1 percent with peak-to-peak swing >= 0.1 V.

TOOL & TECHNOLOGY USED:

Tools and environment: Cadence Virtuoso IC615 (6.1.5), Spectre circuit simulator (MMSIM 12.1), and Assura physical verification (4.1). Process technology is Cadence GPDK045 v6.0 (45 nm generic CMOS), using standard-threshold NMOS devices (g45n1svt, 1.0 V nominal) evaluated across tt, ff, ss, fs, and sf corners.

Device sizing: unit transistors M1-M6 have W = 240 nm, L = 45 nm, and tail transistor M7 has W = 480 nm, L = 90 nm. Device multiplier m scales channel widths in parallel.

Operating conditions: nominal supply VDD = 1 V (varied from 0.9 V to 1.1 V in the process, voltage and temperature (PVT) analysis), nominal temperature 27 C, clock transition times 20 ps, tail bias vb = 1 V, and load capacitance 10 fF per output. Simulations employ 40 ns transient analysis runs in Cadence Spectre.

Virtuoso schematic parameter extraction for the design D DLATCH cell: R1 and R2 = 3 kOhm; M1-M6 W = 240n, L = 45n, m = 4; M7 W = 480n, L = 90n, m = 4. These match Table 2 and the nominal transistor dimensions.

Circuit schematics for the DLATCH and divider core are illustrated in Figure 1 and Figure 2 (ring architecture in Figure 8).

Origin of the figures: the schematic and layout editor views, the Assura DRC summary and the ViVA waveform of design D are screenshots of Cadence tool windows. The other waveforms, sweeps and PVT maps are plots made with Python (matplotlib) from the Spectre result files, and the circuit diagrams are drawn by a script from the netlist. No figure was produced by an image-generation model, and every plotted point comes from a Spectre result file.

SCREENSHOT OF THE SIMULATOR BASED CIRCUIT IMPLEMENTATION:

Unsized baseline (m = 1, R = 8 kOhm): unit devices (m = 1), load R1 = R2 = 8 kOhm, tail bias vb = 1 V, and 1.4 GHz input under nominal conditions (tt corner, 27 C, VDD = 1 V). All eight outputs divide to 700.0 MHz, with Q1 swinging from 0.749 V to 0.978 V.

Selection of R: load resistance was swept from 5 to 12 kOhm at tail bias vb = 0.8 V and 1 V. Division fails up to 6 kOhm and succeeds from 7 kOhm at vb = 1 V; at vb = 0.8 V it fails up to 7 kOhm and divides from 8 kOhm. The value R = 8 kOhm at vb = 1 V was selected as the minimum round value dividing at both biases.

Failure of reference paper sizing: direct implementation of the paper rule (m = 1, R1 = R2 = Ron/2 = 1.15 kOhm, Ron = 2.3 kOhm) fails to divide at 1.4 GHz. Output Q1 oscillates at 2799.8 MHz (2.0 x f_in) with only 15.3 mV swing (Figure 9). Supply power is 0.165 mW; delay, PDP, and phase error are undefined.

Mechanism: the pull-down path comprises three stacked devices (M1, M5, M7) with effective resistance 3 Ron = 6.90 kOhm for m = 1. Regeneration requires R1 >= 1.1 x 3 Ron = 7.59 kOhm as established in Theory, consistent with simulated bounds of 6-7 kOhm at vb = 1 V and 7-8 kOhm at vb = 0.8 V.

Schematic checks: 0 errors and 0 warnings for DLATCH and divider_core; 0 errors and 1 warning for tb_divider (the supply source instance and its net are both named VDD).

Table 1: Device list, circuit without the sizing concept

Device	W	L	Multiplier	Role
M1, M2	240 nm	45 nm	1	sampling pair (differential inputs)
M3, M4	240 nm	45 nm	1	hold pair (cross-coupled regenerative pair)
M5	240 nm	45 nm	1	switch controlled by CK
M6	240 nm	45 nm	1	switch controlled by CKb
M7	480 nm	90 nm	1	tail current source, gate at vb = 1 V
R1, R2	n/a	n/a	n/a	load resistors, 8 kOhm each

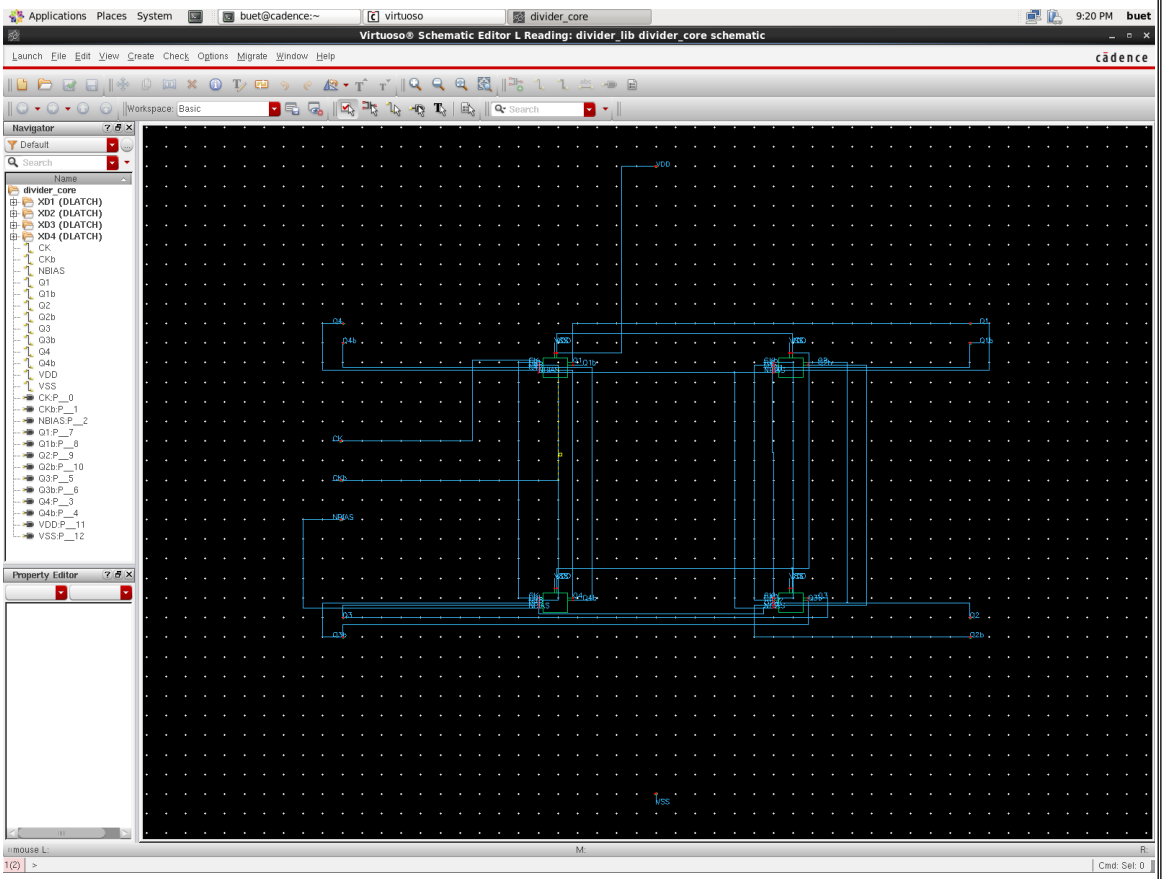


Figure 2: Virtuoso schematic editor window showing the divider core with four DLATCH instances (XD1 to XD4) connected in a ring. The unsized baseline and design D share this topology, differing only in multiplier m and load resistance R (Table 1 and Table 2).

SCREENSHOT OF THE OUTPUT WAVEFORM OBTAINED FROM THE SIMULATOR (DC AND TRANSIENT):

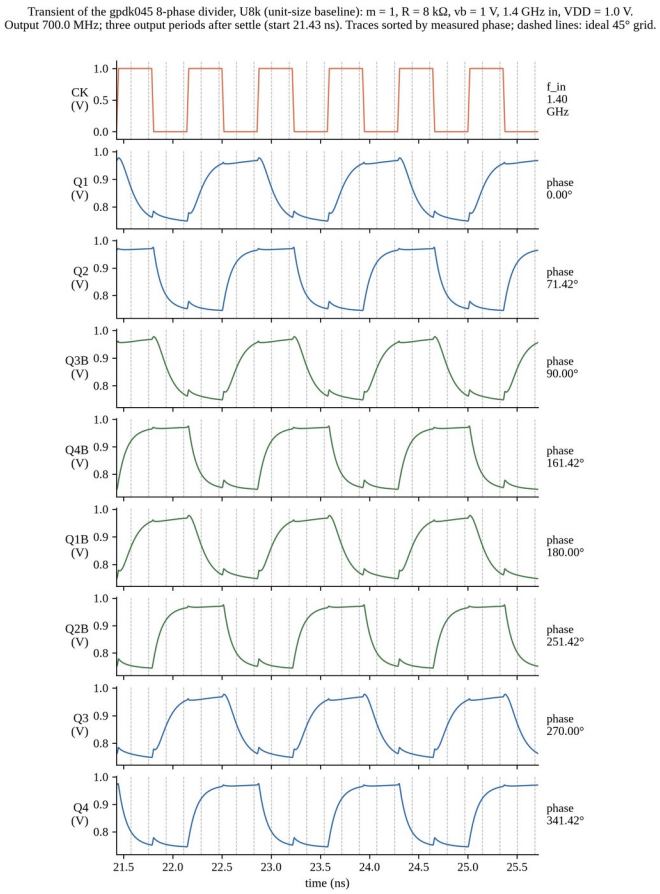


Figure 3: Transient waveforms for the unsized baseline (m = 1, R1 = R2 = 8 kOhm, vb = 1 V) at 1.4 GHz. All eight outputs divide to 700.0 MHz, with Q1 swinging from 0.749 V to 0.978 V. Waveforms for reference paper sizing appear in Figure 9.

Simulation from the Virtuoso schematic

The testbench schematic of the sized divider (design D: R1 = R2 = 3 kOhm, m = 4) was simulated with Spectre directly from Virtuoso at the typical corner (tt, 27 C, VDD = 1.0 V, bias 1.0 V) with a 1.4 GHz input clock. All eight outputs divide to 700 MHz (ratio 2.0). The clock-to-output delay is 26.66 ps and the average supply power is 0.455 mW. Figure 5 shows the corresponding ViVA waveforms.

The standalone netlist of the same circuit gives 0.541 mW and 25.99 ps. The difference comes from the layout-dependent device parameters (stress, well-proximity and series-resistance terms) that the Virtuoso netlister adds to every transistor. Adding the same parameters to the standalone netlist gives 0.455 mW and 26.66 ps, identical to the schematic-driven run. With these parameters the power-delay product of design D is 12.14 fJ instead of 14.07 fJ, and the division is unchanged. The comparative tables in this report use the standalone netlist, which has the default device parameters of the process.

SCREENSHOT OF THE CIRCUIT BASED ON SIZING CONCEPT:

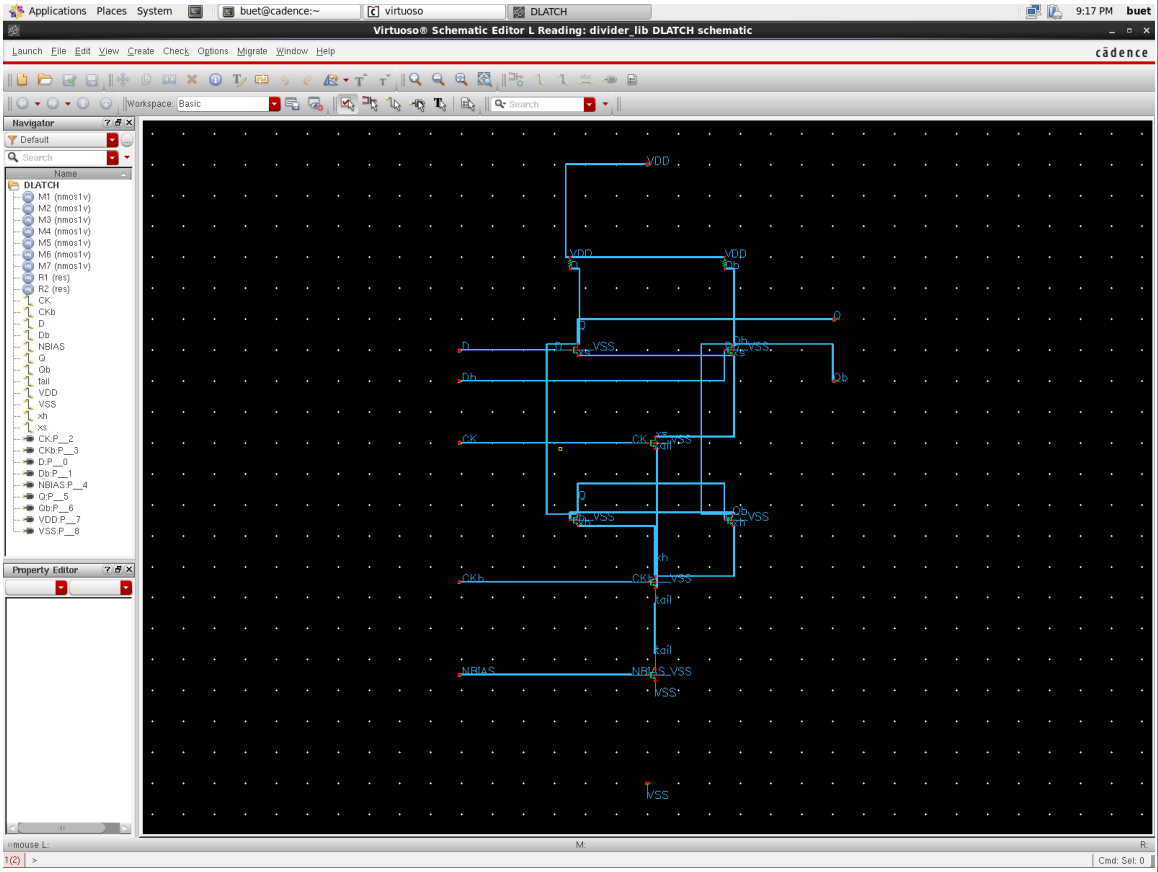


Figure 4: Virtuoso schematic editor window showing the DLATCH cell with sizing applied (design D: m = 4, R1 = R2 = 3 kOhm), consistent with Table 2.

Sized divider (design D): device multiplier m = 4, load R1 = R2 = 3 kOhm, and input 1.4 GHz. The pull-down stack resistance is 3 Ron/m = 1.72 kOhm, requiring load resistance of 1.90 kOhm (tolerance band 1.88 to 2.25 kOhm) according to the stack rule established in Theory. Load R = 3 kOhm provides adequate margin. The same sizing rule applies to design B at 6 GHz (m = 4, R1 = R2 = 2 kOhm). Transistor M7 operates in triode, with transient drain voltage remaining below Vdsat. Figure 4 shows the Virtuoso schematic of the DLATCH cell with this sizing applied, corresponding to the device dimensions listed in Table 2.

Comparison with baseline (Table 3): sizing cuts delay from 62.21 ps (unsized baseline) to 25.99 ps (design D) (2.39x) and increases swing from 0.2289 V to 0.4344 V. Power rises from 0.1375 mW to 0.5413 mW (3.94x), PDP from 8.557 fJ to 14.067 fJ (1.64x), and phase-step error from 26.42 deg to 38.46 deg at 1.4 GHz.

Table 2: Device list, circuit based on the sizing concept

Device	W	L	Multiplier	Role
M1, M2	240 nm	45 nm	4	sampling pair (differential inputs)
M3, M4	240 nm	45 nm	4	hold pair (cross-coupled regenerative pair)
M5	240 nm	45 nm	4	switch controlled by CK
M6	240 nm	45 nm	4	switch controlled by CKb
M7	480 nm	90 nm	4	tail current source, gate at vb = 1 V
R1, R2	n/a	n/a	n/a	load resistors, 3 kOhm each

SCREENSHOT OF THE OUTPUT WAVEFORM OBTAINED FROM THE SIMULATOR FOR THE CIRCUIT WITH SIZING CONCEPT (DC AND TRANSIENT):

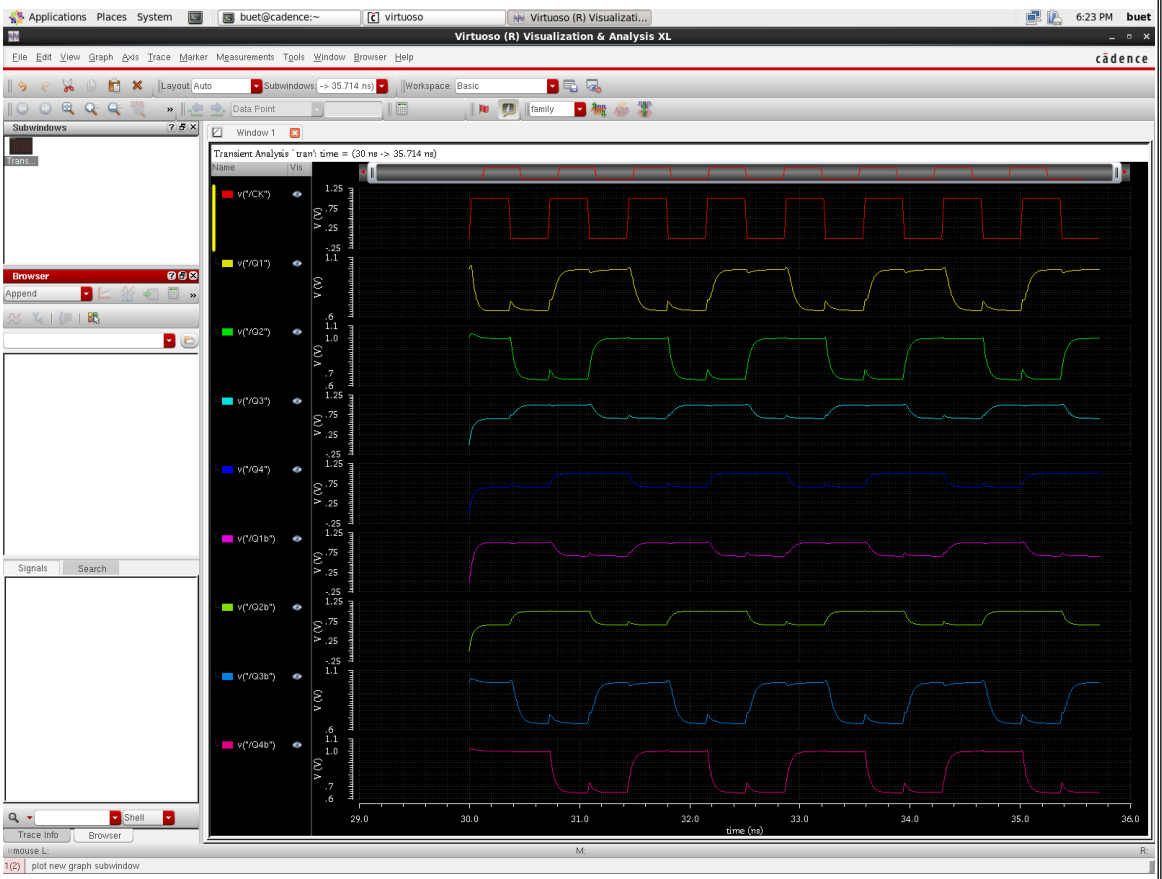


Figure 5: Transient waveforms of design D at 1.4 GHz (tt, 27 C), simulated from the Virtuoso testbench and displayed in the Cadence ViVA waveform viewer.

PROVIDE THE VALUES FOR THE FOLLOWING ALONG WITH THE SCREENSHOTS AS PROOF:

Table 3: Performance values with and without the sizing concept, with the proof figures for each row

Parameter	Value without Sizing	Value with Sizing	Proof (figure)
Power calculation (P)	0.1375 mW	0.5413 mW	Fig. 15 (supply current, both columns)
Delay calculation (t_pd)	62.21 ps	25.99 ps	Calculated mean delay (see note)
Power Delay Product (PDP)	8.557 fJ	14.067 fJ	Calculated: power x delay
Input frequency (f_in)	1.4 GHz	1.4 GHz	Fig. 3 (without), Fig. 5 (with)
Output frequency (f_out)	700.0 MHz	700.0 MHz	Fig. 3 (without), Fig. 5 (with)
Max phase-step error	26.42 deg	38.46 deg	Fig. 11
Output swing	0.2289 V	0.4344 V	Fig. 3 (without), Fig. 5 (with)
Tail-device saturation check (M7)	**Vds = 0.0671 V, Vdsat = 0.3578 V: NOT saturated (triode)**	**Vds = 0.0669 V, Vdsat = 0.3578 V: NOT saturated (triode)**	Fig. 12 (without), Fig. 13 (with)

Notes: Baseline without sizing corresponds to unit devices (unsized baseline: m = 1, R = 8 kOhm, vb = 1 V). Reference paper sizing (m = 1, R = 1.15 kOhm) fails to achieve frequency division (Figure 9). Reported propagation delay denotes multi-phase average delay defined in Theory (single-edge delays are given under transient delay and edge times). Vds indicates peak transient tail node voltage; Vdsat is the extracted saturation voltage for M7.

PDP is computed from unrounded power and delay values.

SCREENSHOT OF THE PVT ANALYSIS:

Table 4: PVT summary for design D at 1.4 GHz (41 of 45 corners pass)

Corner	Temp (°C)	0.9 V	1.0 V	1.1 V
tt	-40	PASS	PASS	PASS
tt	27	PASS	PASS	PASS
tt	125	**FAIL**	PASS	PASS
ff	-40	PASS	PASS	PASS
ff	27	PASS	PASS	PASS
ff	125	PASS	PASS	PASS
ss	-40	PASS	PASS	PASS
ss	27	PASS	PASS	PASS
ss	125	**FAIL**	PASS	PASS
fs	-40	PASS	PASS	PASS
fs	27	PASS	PASS	PASS
fs	125	**FAIL**	PASS	PASS
sf	-40	PASS	PASS	PASS
sf	27	PASS	PASS	PASS
sf	125	**FAIL**	PASS	PASS

Table 5: PVT summary for design B at 6.0 GHz (21 of 45 corners pass)

Corner	Temp (°C)	0.9 V	1.0 V	1.1 V
tt	-40	PASS	PASS	PASS
tt	27	**FAIL**	PASS	PASS
tt	125	**FAIL**	**FAIL**	**FAIL**
ff	-40	PASS	PASS	PASS
ff	27	**FAIL**	PASS	PASS
ff	125	**FAIL**	**FAIL**	**FAIL**
ss	-40	**FAIL**	PASS	PASS
ss	27	**FAIL**	**FAIL**	PASS
ss	125	**FAIL**	**FAIL**	**FAIL**
fs	-40	PASS	PASS	PASS
fs	27	**FAIL**	PASS	PASS
fs	125	**FAIL**	**FAIL**	**FAIL**
sf	-40	**FAIL**	PASS	PASS
sf	27	**FAIL**	**FAIL**	PASS
sf	125	**FAIL**	**FAIL**	**FAIL**

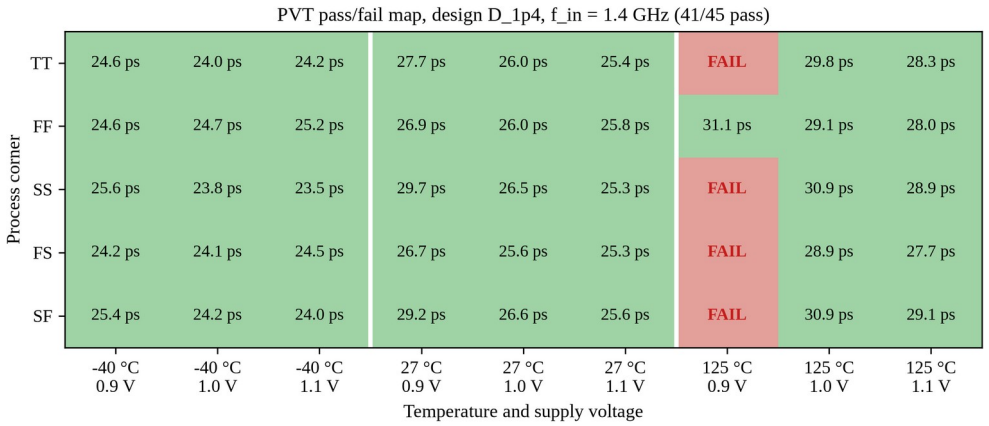


Figure 6: PVT pass/fail map for design D at 1.4 GHz across 5 corners, temperatures -40/27/125 C, and supplies 0.9/1/1.1 V (41 of 45 points pass).

SCREENSHOT OF THE LAYOUT:

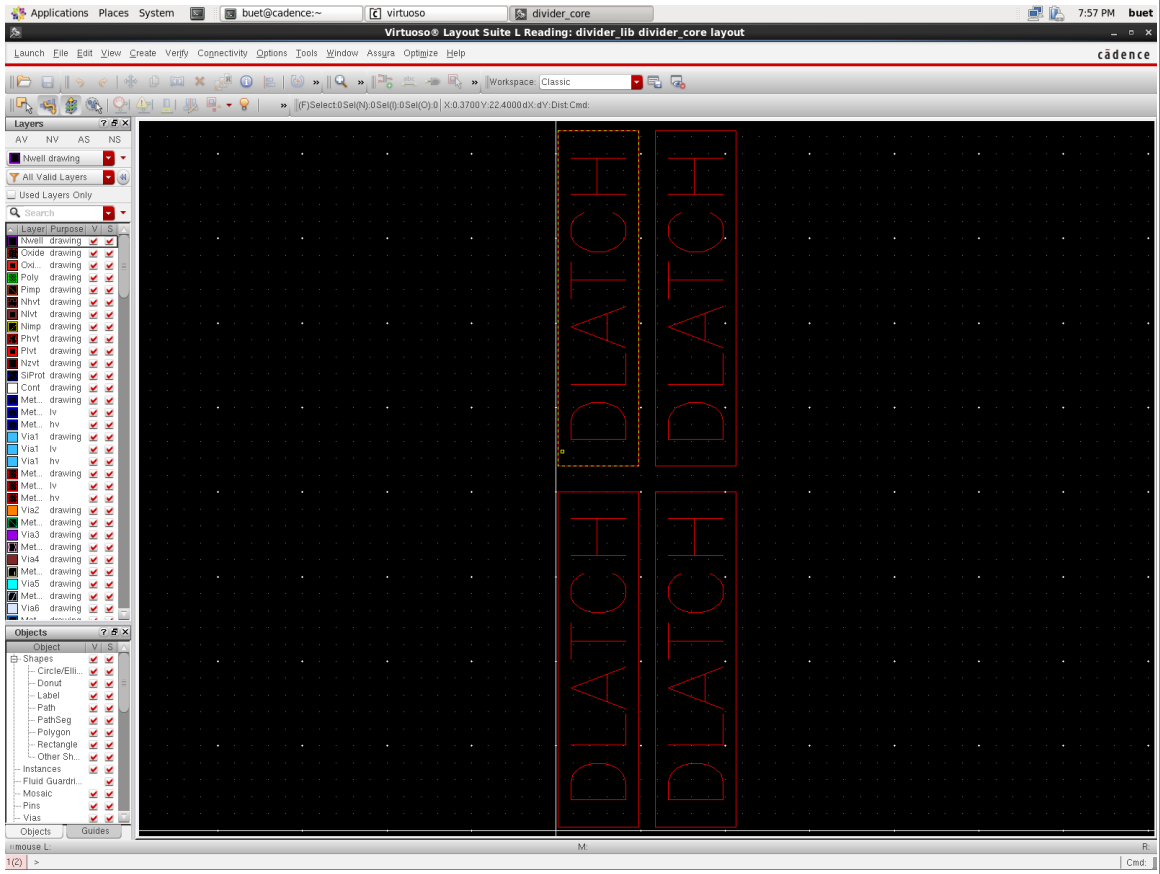


Figure 7: Virtuoso layout editor showing divider_core with four DLATCH instances (XD1 to XD4) placed in a 2x2 array. The layout is placement only, not routed, with no LVS or post-layout simulation; Assura DRC reports 21 errors across 3 rules.

SCREENSHOT OF THE OUTPUT WAVEFORM OBTAINED FROM THE SIMULATOR FOR THE LAYOUT:

No post-layout waveform exists because the layout is placement only.

ANY OTHER RELEVANT INFORMATION:

Layout. The DLATCH cell contains 7 unit NMOS devices (0.595 um wide) and 2 poly resistors (segment width 0.8 um, segment length 7.855 um, 200 ohm/sq, target resistance 2000 ohm). Transistors M1-M6 use 2 fingers of 120 nm (240 nm, L = 45 nm); M7 uses 4 fingers of 120 nm (480 nm, L = 90 nm) for m = 1. Design D requires 4x width (m = 4) and 3 kOhm load (baseline uses 8 kOhm). DLATCH boundary is 4.875 x 20.28 um. Divider core arranges four DLATCH cells in a four-quadrant layout with a 1 um channel between cells. An automatic routing run with Cadence Chip Assembly Router completed 136 of 137 connections but produced 134 DRC errors and mismatches in LVS, so the placement layout is reported. Cell layouts are shown in Figure 7 (divider_core) and Figure 20 (DLATCH).

DRC verification. Assura DRC on DLATCH reports 21 errors across 3 rules (Figure 21). Rules 220 (1) and 221 (6) give 7 substrate-stamp errors from unrouted taps at device pitch 0.755 um. Rule 595 (14) gives 14 Metal1 minimum-area errors (threshold 0.02 um^2) flagged at isolated contact pads. Connected contact pins (0.2 x 0.15 um = 0.03 um^2) meet the minimum area.

Schematic connectivity. Pin-by-pin audit of the 4 DLATCH instances (XD1-XD4) against the netlist confirms exact schematic connectivity with 0 mismatches.

Design B operating point. At 6 GHz (m = 4, R1 = R2 = 2 kOhm), the divider achieves 3000.0 MHz output, 0.4929 mW power, 27.94 ps delay, 13.768 fJ PDP, and 3.78 deg maximum phase error (48.78 and 41.22 deg steps). Output Q1 swings 0.135 V (0.818 V to 0.953 V), above the 0.1 V limit (transient waveforms are shown in Figure 10). Peak tail voltage reaches 66.2 mV, below Vdsat = 357.8 mV (triode, Figure 14). PVT results appear in Table 5.

DC operating points. Prior to clock switching, tail current leakage is negligible (Vgs = 1 V). For reference paper sizing, M7 operates in triode (Vds = 56.3 nV, Ids = 35.6 pA). For design D, M7 operates in triode (Vds = 54.4 nV, Ids = 137.4 pA). For design B (m = 4, vb = 1 V), M7 operates in triode (Vds = 54.4 nV, Ids = 137.4 pA).

Tail transistor operating region. With gate bias Vgs = 1 V and threshold voltage Vth = 527.5 mV, extracted Vdsat is 357.8 mV (at DC initialization, gm = 200.9 pS, gds = 2.531 mS, Vds = 54 nV). In transient operation, the internal tail node voltage spans 8.1 to 66.9 mV for design D (reaching 68.2 mV in the second latch) and 8.0 to 67.1 mV for the unsized baseline. Because Vds remains below Vdsat, M7 operates in triode rather than saturation across all operating conditions (Figures 12 and 13).

Frequency sweeps. Design B (m = 4, R = 2 kOhm) was swept from 1.4 to 6.2 GHz: it divides at 1.4, 2, 3, 4, 5, 5.5, 5.8, 6 GHz and fails at 6.2 GHz. Design D (m = 4, R = 3 kOhm) was swept from 3 to 8 GHz: it divides at 3, 4, 5, 5.5 GHz and fails at 6, 6.5, 7, 8 GHz (the 1.4 GHz operating point also divides). Design E (m = 6, R = 2 kOhm) was swept from 3 to 8 GHz: it divides at 3, 4, 5, 5.5, 6, 6.5, 7 GHz and fails at 8 GHz (1.4 GHz divides at tt, 27 C, 1.0 V). Maximum phase-step error at the highest dividing frequency is 3.78 deg for design B, 13.82 deg for design D, and 15.24 deg for design E, compared with 38.68, 30.89, and 34.32 deg at the lower frequency bounds. In all cases, phase error improves as frequency increases (Figure 16).

Parametric exploration around design B: m = 4, R = 2.2 kOhm divides up to 6.25 GHz (phase error 5.57 deg); m = 4, R = 2.5 kOhm divides up to 6 GHz (phase error 11.23 deg) and fails at 6.25 GHz; m = 5, R = 2.2 kOhm divides up to 6.25 GHz (phase error 16.56 deg); m = 5, R = 2.5 kOhm divides up to 6.25 GHz (phase error 14.36 deg). These sweeps delimit the maximum operating frequency of design B under nominal conditions.

PVT analysis. Across the 45-corner PVT matrix (Table 4 and Table 5), design D fails 4 corners at 1.4 GHz (all at 125 C, 0.9 V), as shown in the pass/fail map in Figure 6; propagation delay and supply power across all corners are plotted in Figure 17. At 1.4 GHz, design B fails 18 corners and design E (m = 6, R = 2 kOhm) fails 4 corners. At 6 GHz, design B fails 24 corners (pass/fail map in Figure 18 and delay/power distribution in Figure 19). Passing corners of design D span from 0.246 to 1.078 mW and 23.54 to 31.05 ps. In Table 6 (Appendix), the Divides column confirms pass and fail status across all 45 corners.

Transient delay and edge times. First-edge CK-to-Q1 delays are 135.96 ps (unsized baseline), 51.95 ps (design D), and 66.10 ps (design B). Multi-phase average delay for design D is 25.99 ps. Output Q1 rise and fall times are 134.6 ps and 102.6 ps. Transient waveforms from the standalone netlist simulation of design D are shown in Figure 22.

Supply current. Average and peak supply currents for design D are 0.541 mA and 0.560 mA, respectively (Figure 15).

Comparison with reference literature. Reported values from Kuo et al. (TSMC 180 nm, 1.8 V, 1.4 GHz) are 2.34 mW, phase error within 3.75 deg, and core area 91.7 x 52.9 um^2. In 45 nm, design D at 1.4 GHz consumes 0.5413 mW with 38.46 deg phase error; design B reaches 3.78 deg at 6 GHz.

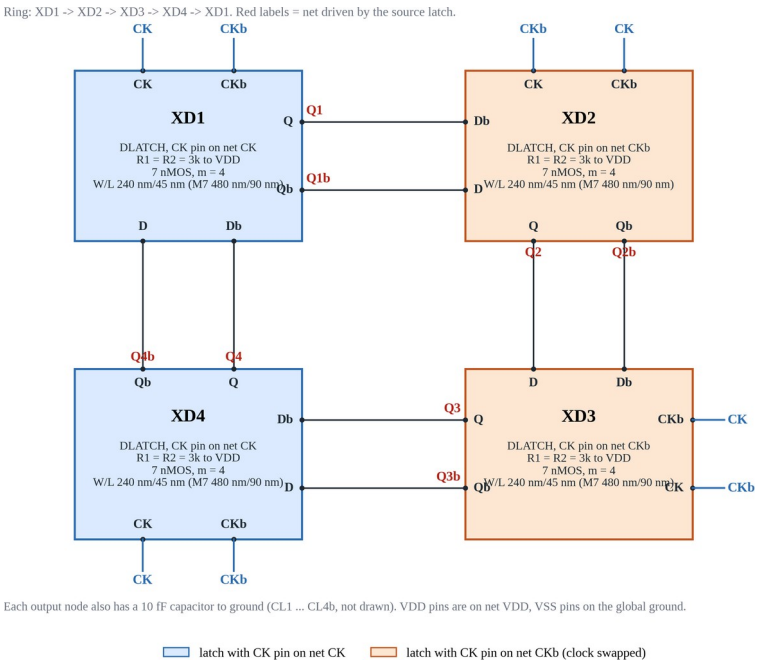


Figure 8: Ring interconnection of four DLATCH stages (XD1 to XD4) with alternating cross-connections, and inverted clocks on XD2 and XD3 (design D: m = 4, R = 3 kOhm).

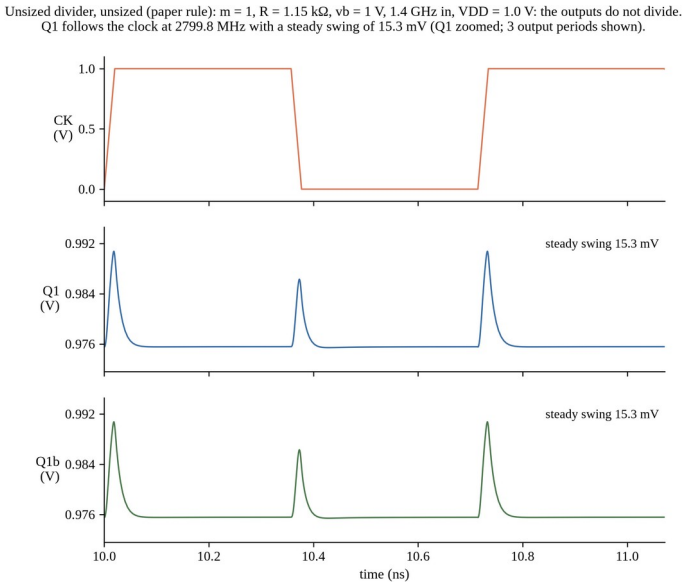


Figure 9: Transient simulation waveforms for reference paper sizing (m = 1, R1 = R2 = 1.15 kOhm = Ron/2) at 1.4 GHz, showing failure to divide.

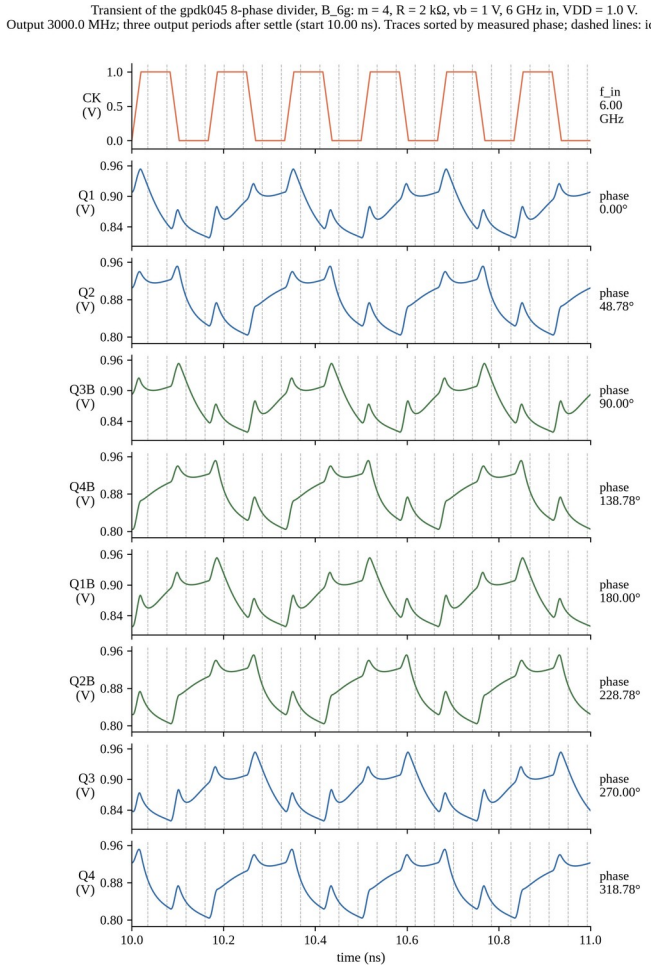


Figure 10: Transient waveforms for design B at 6 GHz (m = 4, R1 = R2 = 2 kOhm), yielding divided outputs at 3000.0 MHz.

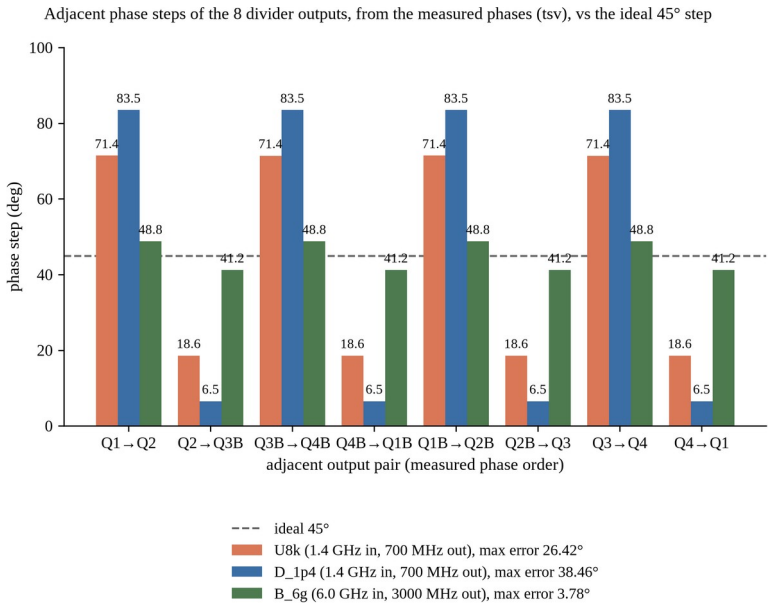


Figure 11: Phase steps between the eight outputs for unsized baseline (1.4 GHz), design D (1.4 GHz), and design B (6 GHz).

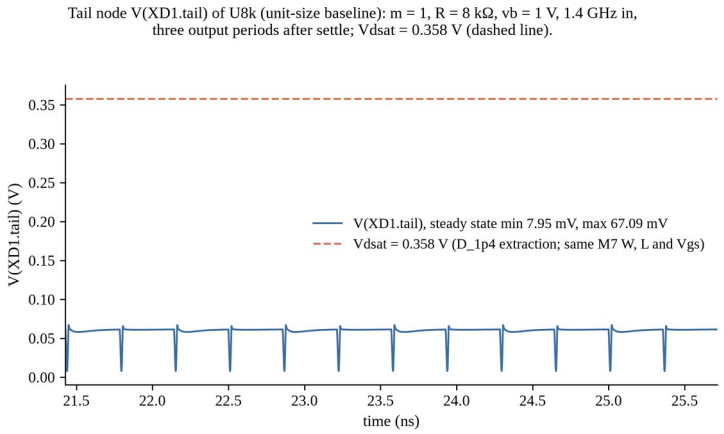


Figure 12: Tail transistor (M7) drain voltage for unsized baseline compared with saturation voltage Vdsat = 0.358 V.

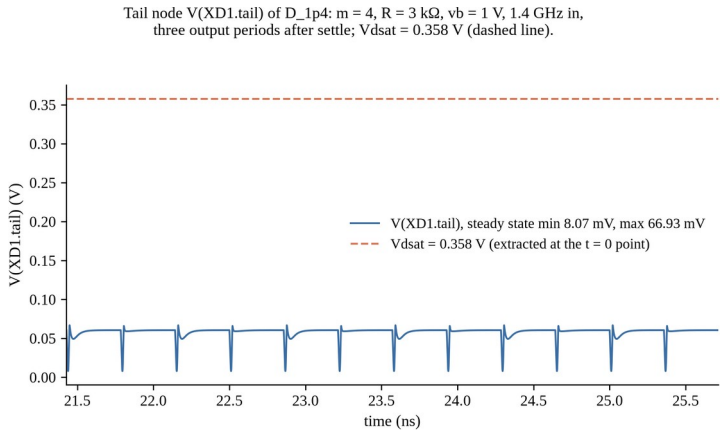


Figure 13: Tail transistor (M7) drain voltage for design D at 1.4 GHz compared with saturation voltage Vdsat = 0.358 V.

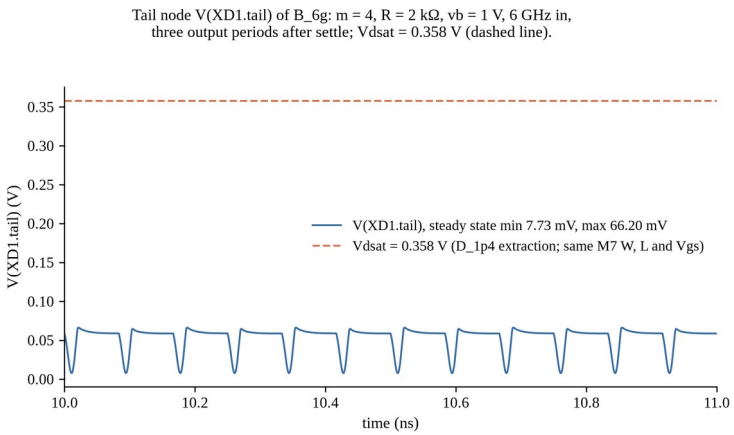


Figure 14: Tail transistor (M7) drain voltage for design B at 6 GHz compared with saturation voltage Vdsat = 0.358 V.

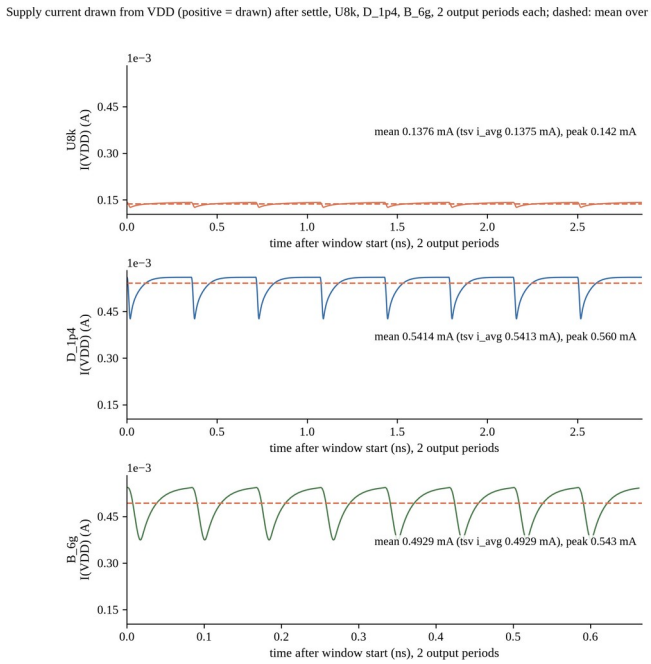


Figure 15: Supply current drawn from VDD for unsized baseline, design D, and design B.

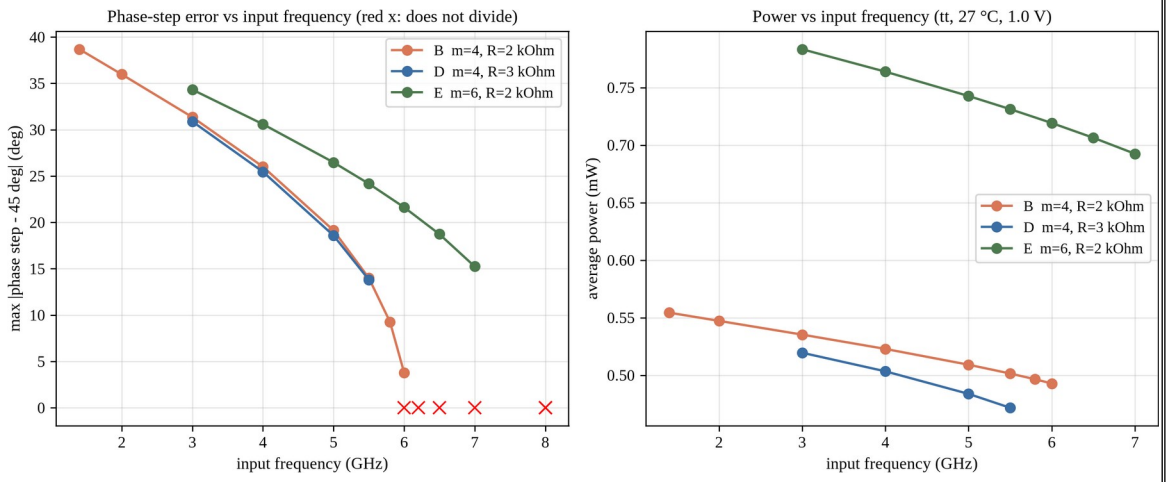


Figure 16: Frequency sweeps for designs B, D, and E showing division range and maximum phase-step error versus input frequency.


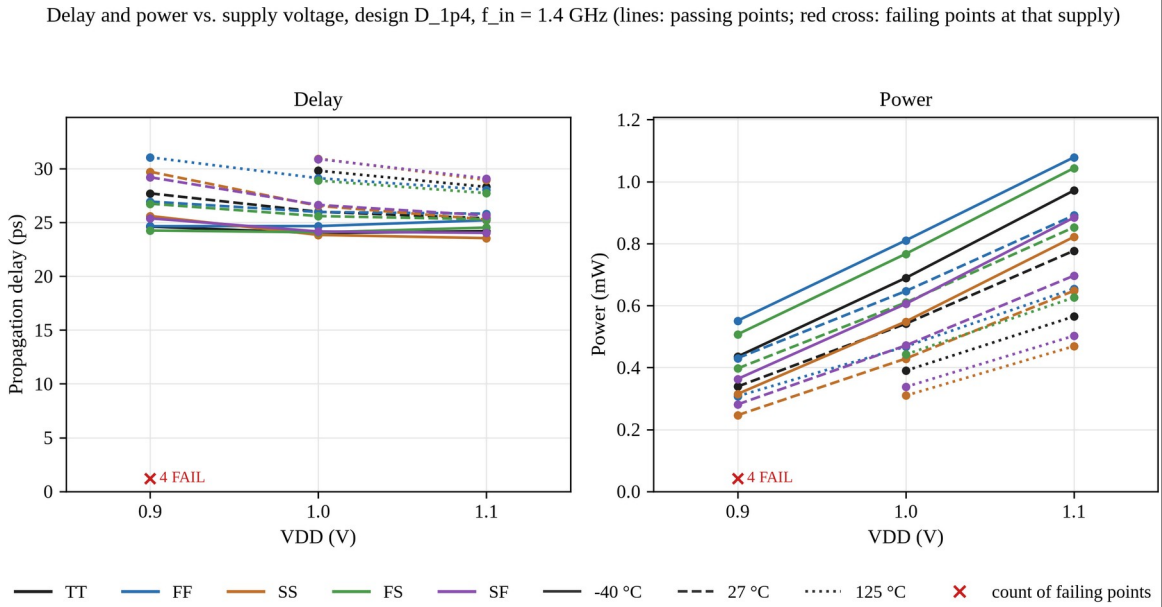


Figure 17: Delay and power across the PVT matrix for design D at 1.4 GHz (crosses mark failing corners).

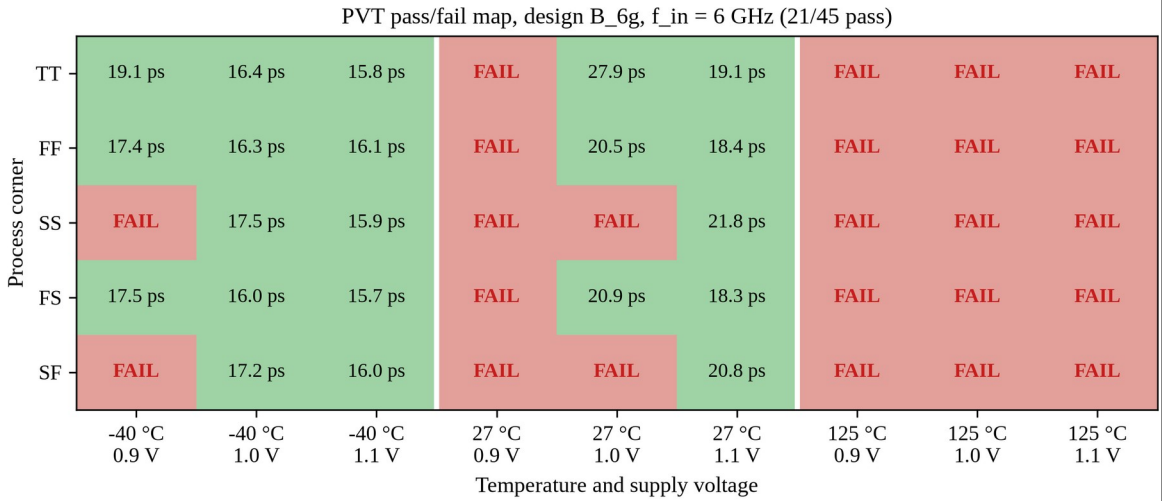

Green: pass, cell text is propagation delay. Red: FAIL (wrong divide ratio or output not toggling).

Figure 18: PVT pass/fail map for design B at 6 GHz (21 of 45 points pass).

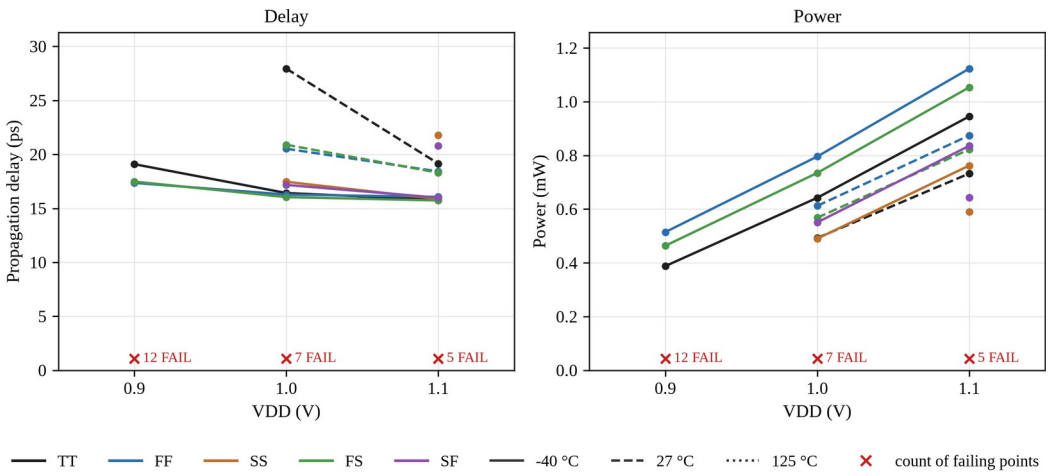


Figure 19: Delay and power across the PVT matrix for design B at 6 GHz (crosses mark failing corners).

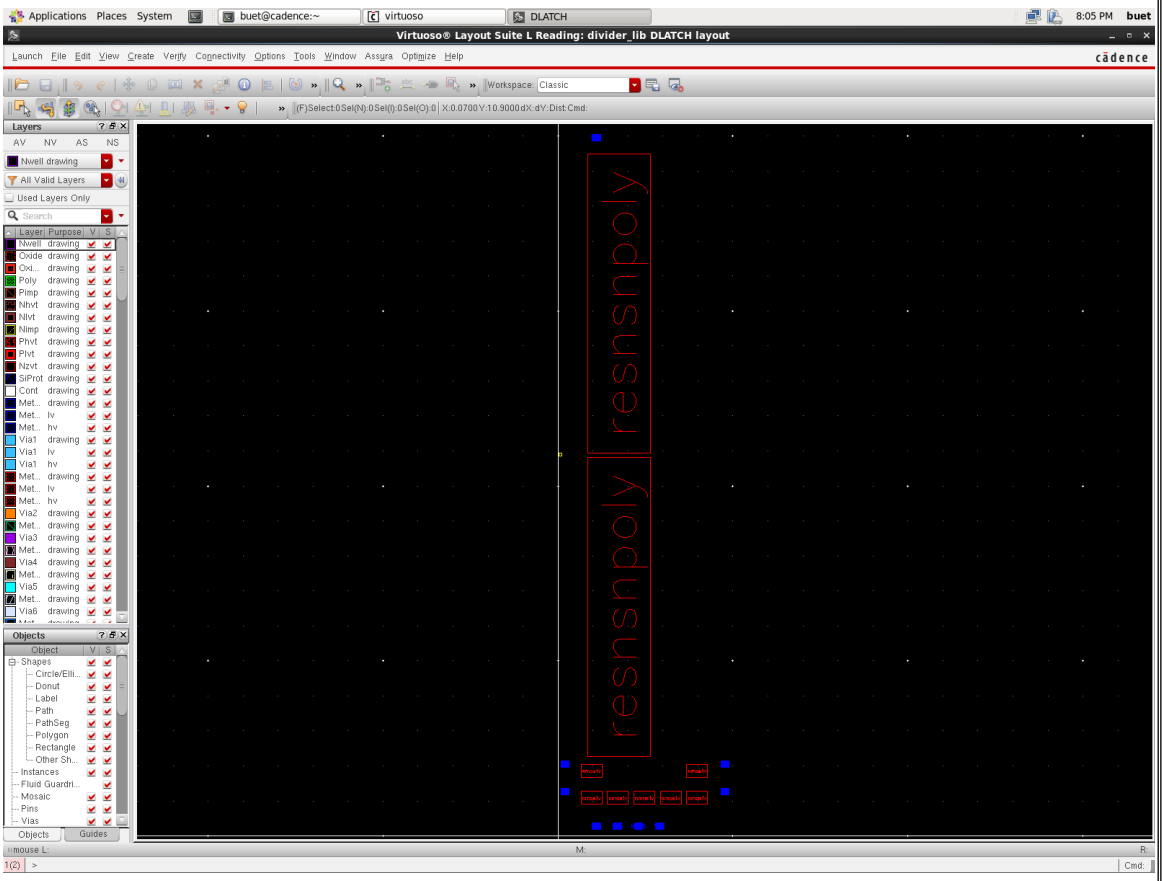


Figure 20: Virtuoso layout editor showing the DLATCH cell: 7 unit NMOS devices (m = 1) and 2 poly resistors.

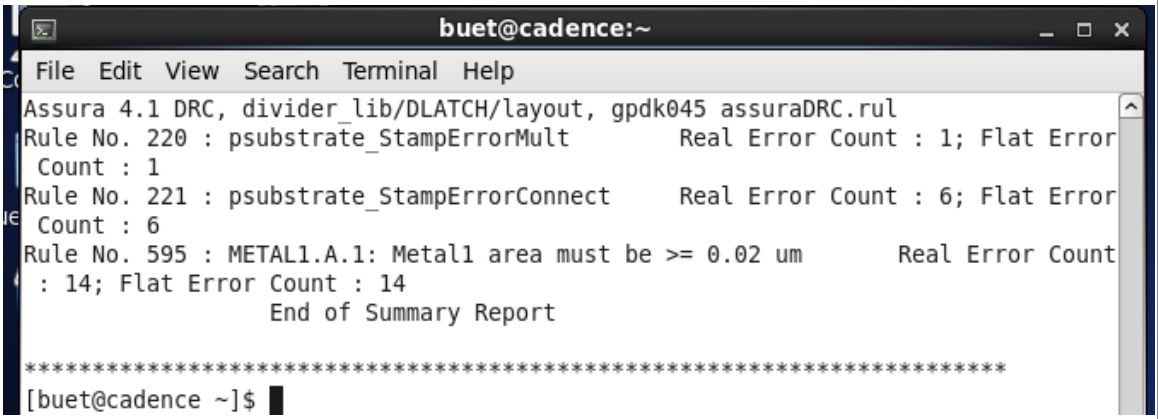


Figure 21: Assura DRC summary for the DLATCH layout showing 21 errors across 3 rules.

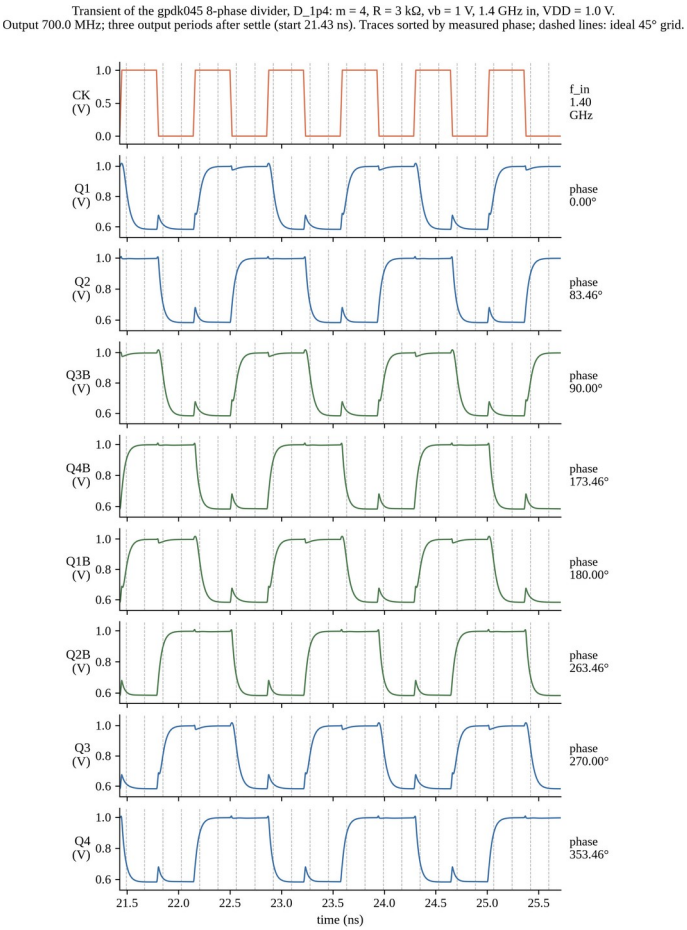


Figure 22: Transient waveforms for design D (m = 4, R1 = R2 = 3 kOhm) at 1.4 GHz. Output frequency is 700.0 MHz with Q1 swinging from 0.583 V to 1.017 V.

CONCLUSION:

Multiphase CMOS division in 45 nm is demonstrated for design D at 1.4 GHz (41 of 45 PVT corners passing) and design B at 6 GHz (21 of 45 PVT corners passing). Device sizing significantly reduces propagation delay and increases voltage swing at the expense of higher power dissipation (Table 3).

Reference paper sizing fails to divide because load resistance falls below the stack regeneration threshold.

Operating limitations: tail transistor M7 operates in triode across all designs due to low transient drain headroom. All PVT failures for design D are confined to the slow-supply corner (125 C, 0.9 V). Design B achieves low phase error (3.78 deg) matching the literature benchmark, but exhibits reduced swing (0.135 V) and fails division beyond 6 GHz.

Physical implementation was evaluated as an unrouted placement with 21 documented Assura DRC errors across 3 rules; routing, LVS, and post-layout simulation were not performed.

PROBLEMS FACED DURING THE IMPLEMENTATION:

The reference paper sizing rule failed to divide at unit device size because load resistance fell below the regeneration threshold.

Conventional division checks initially counted false passes caused by low-amplitude harmonics at 2 f_in.

Tail current source transistor M7 operated in triode rather than saturation due to limited drain voltage headroom.

Spectre BSIM4 model compilation failed on the 32-bit simulation host due to missing compiler and runtime libraries.

Automated routing of the divider core produced DRC errors and LVS mismatches.

PROBLEMS RESOLVED USING SOLUTIONS:

Resized load resistance using the 3 Ron/m stack regeneration rule, selecting R = 8 kOhm for the unsized baseline and R = 3 kOhm for design D.

Introduced an eight-output verification check requiring division to f_in/2 within 0.1% and output swing >= 0.1 V across all outputs.

Characterized transient tail node voltages against extracted BSIM4 Vdsat, confirming triode operation.

Installed the missing compiler and runtime libraries to enable native 32-bit Spectre model compilation.

Reported the placement layout with its DRC result, because the automatic router output carried 134 DRC errors and LVS mismatches.

ANY OTHER COMMENT:

The power and PDP in Table 3 come from the standalone netlist with default device parameters (transient waveforms in Figure 22); the schematic-driven run, which includes the layout-dependent parameters, gives lower power (see the schematic-simulation discussion). Post-layout simulation was not possible because the process kit provides no parasitic-extraction rule files.

REFERENCES:

Yue-Fang Kuo, Shih-Hung Lin, Bo-Yi Chen and Liang-Chen Liu, "A Compact Multiphase Divide-by-Two CMOS Frequency Divider," IEEE Microw. Wireless Technol. Lett., vol. 35, no. 5, pp. 617-620, May 2025, doi: 10.1109/LMWT.2025.3528863.

Cadence Design Systems, Cadence GPDK045 v6.0 documentation (45 nm generic process design kit).

Cadence Design Systems, Spectre Circuit Simulator Reference, MMSIM 12.1.

APPENDIX: COMPLETE PVT DATA

Complete 45-corner simulation results for design D at 1.4 GHz across process corners (tt, ff, ss, fs, sf), temperatures (-40, 27, 125 °C), and supply voltages (0.9, 1.0, 1.1 V). Total 41 corners pass division to 700.0 MHz; 4 corners fail (all at 125 °C, 0.9 V for tt, ss, fs, sf).

Table 6: Complete PVT analysis results for design D at 1.4 GHz (45 corners)

Corner	Temp (°C)	VDD (V)	Divides	f_out (MHz)	Delay (ps)	Power (mW)	PDP (fJ)	Note
tt	-40	0.9	PASS	700.0	24.61	0.4356	10.72	
tt	-40	1.0	PASS	700.0	24.01	0.6892	16.54	
tt	-40	1.1	PASS	700.0	24.19	0.9714	23.50	
tt	27	0.9	PASS	700.0	27.70	0.3387	9.38	
tt	27	1.0	PASS	700.0	25.99	0.5413	14.07	
tt	27	1.1	PASS	700.0	25.38	0.7769	19.72	
tt	125	0.9	**FAIL**	2799.7	n/a	n/a	n/a	outputs at 2 f_in, swing 0.034 V < 0.1 V
tt	125	1.0	PASS	700.0	29.81	0.3898	11.62	
tt	125	1.1	PASS	700.0	28.30	0.5648	15.98	
ff	-40	0.9	PASS	700.0	24.65	0.5512	13.59	
ff	-40	1.0	PASS	700.0	24.66	0.8104	19.99	
ff	-40	1.1	PASS	700.0	25.20	1.0784	27.17	
ff	27	0.9	PASS	700.0	26.94	0.4303	11.59	
ff	27	1.0	PASS	700.0	25.97	0.6467	16.80	
ff	27	1.1	PASS	700.0	25.81	0.8910	23.00	
ff	125	0.9	PASS	700.0	31.05	0.3074	9.55	
ff	125	1.0	PASS	700.0	29.11	0.4677	13.61	
ff	125	1.1	PASS	700.0	28.04	0.6547	18.36	
ss	-40	0.9	PASS	700.0	25.60	0.3147	8.06	
ss	-40	1.0	PASS	700.0	23.84	0.5483	13.07	
ss	-40	1.1	PASS	700.0	23.54	0.8217	19.34	
ss	27	0.9	PASS	700.0	29.71	0.2463	7.32	
ss	27	1.0	PASS	700.0	26.54	0.4288	11.38	
ss	27	1.1	PASS	700.0	25.27	0.6476	16.37	

Corner	Temp (°C)	VDD (V)	Divides	f_out (MHz)	Delay (ps)	Power (mW)	PDP (fJ)	Note
ss	125	0.9	**FAIL**	2799.7	n/a	n/a	n/a	outputs at 2 f_in, swing 0.029 V < 0.1 V
ss	125	1.0	PASS	700.0	30.93	0.3095	9.57	
ss	125	1.1	PASS	700.0	28.94	0.4688	13.57	
fs	-40	0.9	PASS	700.0	24.25	0.5072	12.30	
fs	-40	1.0	PASS	700.0	24.08	0.7669	18.46	
fs	-40	1.1	PASS	700.0	24.52	1.0436	25.59	
fs	27	0.9	PASS	700.0	26.74	0.3971	10.62	
fs	27	1.0	PASS	700.0	25.59	0.6098	15.61	
fs	27	1.1	PASS	700.0	25.29	0.8525	21.56	
fs	125	0.9	**FAIL**	700.0	n/a	n/a	n/a	divides, swing 0.093 V < 0.1 V
fs	125	1.0	PASS	700.0	28.89	0.4423	12.78	
fs	125	1.1	PASS	700.0	27.72	0.6259	17.35	
sf	-40	0.9	PASS	700.0	25.38	0.3632	9.22	
sf	-40	1.0	PASS	700.0	24.16	0.6055	14.63	
sf	-40	1.1	PASS	700.0	24.03	0.8837	21.23	
sf	27	0.9	PASS	700.0	29.20	0.2811	8.21	
sf	27	1.0	PASS	700.0	26.63	0.4713	12.55	
sf	27	1.1	PASS	700.0	25.65	0.6964	17.86	
sf	125	0.9	**FAIL**	2799.7	n/a	n/a	n/a	outputs at 2 f_in, swing 0.031 V < 0.1 V
sf	125	1.0	PASS	700.0	30.89	0.3375	10.43	
sf	125	1.1	PASS	700.0	29.09	0.5023	14.61	